

Logic Design

CPSC 235 - Computer Organization

References

- Slides adapted from CMU

Outline

- Introduction to binary logic gates
- Truth table construction
- Logic functions and their simplifications
- Laws of binary logic

Overview of Logic Design

- Fundamental Hardware Requirements
 - Communication (how to get values from one place to another)
 - Computation
 - Storage
- Bits
 - Everything expressed in terms of values 0 and 1
 - Communication: low or high voltage on wire
 - Computation: compute with Boolean functions
 - Storage: store bits of information

Digital Signals

- Use voltage thresholds to extract discrete values from continuous signal.
- Simplest version: 1-bit signal
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small and fast

Semiconductors to Computers

- Increasing levels of complexity
 - Transistors built from semiconductors
 - Logic gates built from transistors
 - Logic functions built from gates
 - Flip-flops built from logic
 - Counters and sequencers from flip-flops
 - Microprocessors from sequencers
 - Computers from microprocessors

Semiconductors to Computers

- Increasing levels of Abstraction
 - Physics
 - Transistors
 - Gates (this lecture)
 - Logic (this lecture)
 - Microprogramming
 - Assembler
 - Programming languages
 - Applications


Logic Gates

- Basic logic circuits with one or more inputs and one output are called gates
- Gates are used as the building blocks in the design of more complex digital logic circuits.

Representing Logic Functions

- There are several ways of representing logic functions:
 - Symbols to represent the gates
 - Truth tables
 - Boolean algebra

NOT Gate

 


■ Truth table

<u>a</u>	<u>y</u>
0	1
1	0

■ Boolean algebra

$$y = \bar{a}$$

AND Gate

 


■ Truth table

<u>a</u>	<u>b</u>	<u>y</u>
0	0	0
0	1	0
1	0	0
1	1	1

■ Boolean algebra

$$y = a \cdot b$$

OR Gate

 


■ Truth table

<u>a</u>	<u>b</u>	<u>y</u>
0	0	0
0	1	1
1	0	1
1	1	1

■ Boolean algebra

$$y = a + b$$

XOR Gate

 


■ Truth table

<u>a</u>	<u>b</u>	<u>y</u>
0	0	0
0	1	1
1	0	1
1	1	0

■ Boolean algebra

$$y = a \oplus b$$

NOT AND (NAND) Gate

 


■ Truth table

<u>a</u>	<u>b</u>	<u>y</u>
0	0	1
0	1	1
1	0	1
1	1	0

■ Boolean algebra

$$y = \overline{a \cdot b}$$

NOT OR (NOR) Gate

 

■ Truth table

<u>a</u>	<u>b</u>	<u>y</u>
0	0	1
0	1	0
1	0	0
1	1	0

■ Boolean algebra

$$y = \overline{a + b}$$

Boolean Algebra

- Boolean algebra can be used to design combinational logic circuits

- OR

- $a + 0 = a$

- $a + a = a$

- $a + 1 = 1$

- $a + \bar{a} = 1$

- AND

- $a \cdot 0 = 0$

- $a \cdot a = a$

- $a \cdot 1 = a$

- $a \cdot \bar{a} = 0$

Boolean Algebra Properties

■ Commutation

- $a + b = b + a$

- $a \cdot b = b \cdot a$

■ Association

- $(a + b) + c = a + (b + c)$

- $(a \cdot b) \cdot c = a \cdot (b \cdot c)$

■ Distribution

- $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

- $a + (b \cdot c) = (a + b) \cdot (a + c)$

■ Absorption

- $a + (a \cdot c) = a$

- $a \cdot (a + c) = a$

Boolean Algebra Example

- Simplify

$$x \cdot y \cdot z + x \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{y} \cdot z$$

$$x \cdot y \cdot (z + \bar{z}) + \bar{y} \cdot z \cdot (x + \bar{x})$$

$$x \cdot y \cdot 1 + \bar{y} \cdot z \cdot 1$$

$$x \cdot y + \bar{y} \cdot z$$

DeMorgan's Theorem

- $\overline{a + b + c + \dots} = \bar{a} \cdot \bar{b} \cdot \bar{c} \cdot \dots$
- $\overline{a \cdot b \cdot c \cdot \dots} = \bar{a} + \bar{b} + \bar{c} + \dots$
- Proof for $\overline{a + b} = \bar{a} \cdot \bar{b}$

a	b	$\overline{a + b}$	$\bar{a} \cdot \bar{b}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

DeMorgan's Example

- Simplify

$$a \cdot \bar{b} + a \cdot (\overline{b + c}) + b \cdot (\overline{b + c})$$


$$a \cdot \bar{b} + a \cdot \bar{b} \cdot \bar{c} + b \cdot \bar{b} \cdot \bar{c}$$

$$a \cdot \bar{b} + a \cdot \bar{b} \cdot \bar{c}$$

$$a \cdot \bar{b}$$


DeMorgan's in Gates

 - The function $f = a \cdot b + c \cdot d$ can be implemented with AND and OR gates




DeMorgan's in Gates

- Two consecutive NOT gates cancel out.

 

DeMorgan's in Gates

 - The function $f = a \cdot b + c \cdot d$ can be simplified to use only NAND gates.



Logic Minimisation

- Any Boolean function can be implemented directly using combinational logic
- Simplifying the Boolean function will reduce the number of gates required to implement the function
- Logic minimization techniques:
 - Algebraic manipulation
 - Karnaugh (K) mapping (visual approach)
 - Tabular approaches (for example Quine-McCluskey)
- Karnaugh mapping is usually preferred for up to about 5 variables

Truth Tables

- f is defined by the following truth table

x	y	z	f	minterms
0	0	0	1	$\bar{x} \cdot \bar{y} \cdot \bar{z}$
0	0	1	1	$\bar{x} \cdot \bar{y} \cdot z$
0	1	0	1	$\bar{x} \cdot y \cdot \bar{z}$
0	1	1	1	$\bar{x} \cdot y \cdot z$
1	0	0	0	
1	0	1	0	
1	1	0	0	
1	1	1	1	$x \cdot y \cdot z$

- A minterm must contain all variables (in either complemented or uncomplemented form)

Disjunctive Normal Form

- A Boolean function expressed as the disjunction (OR) of its minterms is said to be in the Disjunctive Normal Form (DNF)
- Example:

$$f = \bar{x} \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot \bar{z} + \bar{x} \cdot y \cdot z + x \cdot y \cdot z$$

- A Boolean function expressed as the ORing of ANDed variables (not necessarily minterms) is in Sum of Products (SOP) form.

$$f = \bar{x} + y \cdot z$$

Maxterms

- A maxterm of n Boolean variables is the disjunction of all the variables either in complemented or uncomplemented form.
- Example (referring to the truth table for f)

$$\bar{f} = x \cdot \bar{y} \cdot \bar{z} + x \cdot \bar{y} \cdot z + z \cdot y \cdot \bar{z}$$

$$f = (\bar{x} + y + z) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

- The maxterms of f are effectively the minterms of \bar{f} with each variable complemented.

Conjunctive Normal Form

- A Boolean function expressed as the conjunction (AND) of its maxterms is said to be in Conjunctive Normal Form (CNF)
- Example:

$$f = (\bar{x} + y + z) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

- A Boolean function expressed as the ANDing of ORed variables (not necessarily maxterms) is often said to be in Product of Sums (POS) form.

Logic Simplification

- Boolean algebra can be used to simplify logical expressions.
- Note: the DNF and CNF are not simplified
- There is a technique called Karnaugh mapping that is sometimes easier (for humans to do)

Karnaugh Maps

- Karnaugh Maps (or K-maps) are a powerful visual tool for carrying out simplification and manipulation of logical expressions with less than 6 variables.
- The K-map is a rectangular array of cells
 - Each possible state of the input variables corresponds uniquely to one of the cells
 - The corresponding output state is written in each cell

K-map Example

- Simplify:

$$f = \bar{x} \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot \bar{z} + \bar{x} \cdot y \cdot z + x \cdot y \cdot z$$

- K-map:

x

z

$f(x, y, z)$

	000	001	101	100
	1	1	0	0
y	010	011	111	110
	1	1	1	0

K-map Example

- Group terms
 - With size equal to a power of 2
 - Large groups best since they contain fewer variables
 - Groups can wrap around edges and corners

x

$f(x, y, z)$

	z			
	000	001	101	100
	1	1	0	0
y	010	011	111	110
	1	1	1	0

- Simplified: $f = \bar{x} + y \cdot z$

K-map Example

- Plot $f = \bar{a} \cdot b + b \cdot \bar{c} \cdot \bar{d}$

$f(a, b, c, d)$

0000 0	0001 0	0101 1	0100 1
0010 0	0011 0	0111 1	0110 1
1010 0	1011 0	1111 0	1110 0
1000 0	1001 0	1101 0	1100 1

- In a 4 variable map:
 - 1 variable term occupies 8 cells
 - 2 variable terms occupy 4 cells
 - 3 variable terms occupy 2 cells, etc.

K-map Example

- Plot $f = \bar{b}$

b

$f(a, b, c, d)$

d

0000	0001	0101	0100
1	1	0	0
0010	0011	0111	0110
1	1	0	0
1010	1011	1111	1110
1	1	0	0
1000	1001	1101	1100
1	1	0	0

a

c

K-map Example

- Plot $f = \bar{b} \cdot \bar{d}$

b

$f(a, b, c, d)$

d

0000	0001	0101	0100
1	0	0	0
0010	0011	0111	0110
1	0	0	0
1010	1011	1111	1110
1	0	0	0
1000	1001	1101	1100
1	0	0	0

a

c

K-map Example

- Simplify $f = \bar{a} \cdot \bar{b}d + b \cdot c \cdot d + \bar{a} \cdot b \cdot \bar{c} \cdot d + c \cdot d$

$f(a, b, c, d)$

		----- b			
		----- d			
		0000	0001	0101	0100
		0	0	1	1
	----- c	0010	0011	0111	0110
		0	1	1	1
----- a	1010	1011	1111	1110	
	0	1	1	0	
	1000	1001	1101	1100	
	0	0	0	0	

- $f = \bar{a} \cdot b + c \cdot d$

POS Simplification

- Note that the previous examples yielded simplified expressions in the SOP form
 - Suitable for implementations using AND followed by OR gates, or only NAND gates
- Sometimes we may wish to get a simplified expression in POS form
 - Suitable for implementations using OR followed by AND gates, or only NOR gates
- To do this we group zeros in the map, then apply DeMorgan's and complement

POS Example

- Simplify $f = \bar{a} \cdot b + b \cdot \bar{c} \cdot \bar{d}$ into POS form

$f(a, b, c, d)$

		b		
		d		
	0000	0001	0101	0100
	0	0	1	1
	0010	0011	0111	0110
	0	0	1	1
c	1010	1011	1111	1110
	0	0	0	0
a	1000	1001	1101	1100
	0	0	0	1

- Simplified: $\bar{f} = \bar{b} + a \cdot c + a \cdot d$
- Applying DeMorgan's: $f = b \cdot (\bar{a} + \bar{c}) \cdot (\bar{a} + \bar{d})$

Expressions in POS Form

- Apply DeMorgan's and take the complement, that is, \bar{f} is now in SOP form
- Fill in zeros in table, that is, plot \bar{f}
- Fill remaining cells with ones, that is, plot f
- Simplify in the usual way by grouping ones to simplify f

Don't Care Conditions

- Sometimes we do not care about the output value of a combinational logic circuit, for example, if certain input combinations can never occur.
- These are called don't care conditions
- In a simplification they may be treated as 0 or 1 depending on which gives the simplest result

Don't Care Conditions Example

- Simplify the function $f = \bar{a} \cdot \bar{b} \cdot d + \bar{a} \cdot c \cdot d + a \cdot c \cdot d$ with don't care conditions $\bar{a} \cdot \bar{b} \cdot \bar{c} \cdot \bar{d}$, $\bar{a} \cdot \bar{b} \cdot c \cdot \bar{d}$, $\bar{a} \cdot b \cdot \bar{c} \cdot d$

$\overbrace{\hspace{2cm}}^b$

$f(a, b, c, d)$


		$\overbrace{\hspace{2cm}}^d$			
		0000	0001	0101	0100
		-	1	-	0
	$\overbrace{\hspace{1cm}}^c$	0010	0011	0111	0110
		-	1	1	0
		1010	1011	1111	1110
		0	1	1	0
$\overbrace{\hspace{1cm}}^a$		1000	1001	1101	1100
		0	0	0	0

- Simplified: $f = \bar{a} \cdot \bar{b} + c \cdot d$ or $f = \bar{a} \cdot d + c \cdot d$

K-map Definitions

- Cover - a term is said to cover a minterm if that minterm is part of that term
- Prime implicant - a term that cannot be further combined
- Essential term - a prime implicant that covers a minterm that no other prime implicant covers
- Covering set - a minimum set of prime implicants which includes all essential terms plus any other prime implicants required to cover all minterms

Combinational Circuit Example

 

■ Truth table

<i>a</i>	<i>b</i>	<i>out</i>
0	0	1
0	1	0
1	0	0
1	1	1

Half Adder

- Adds two single bit binary numbers a and b (note: no carry input)
- Truth table

a	b	c_{out}	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Full adder

- Adds two single bit numbers a and b (note: with a carry input)
- Truth table

c_{in}	a	b	c_{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Ripple Carry Adder

 - The half adder and full adder implement two bit binary addition with and without carry-in
- In general, we need to add two n bit binary numbers
- The ripple carry adder is n full adders cascaded together.
- Example: 4 bit adder




- Note: if a is complemented and c_0 set to 1, then the operation is: $s = b - a$

Bit-Level Multiplexor

- A bit-level multiplexor has data signals a and b and a control signal c outputs a or b depending on c
- Truth table


a	b	c	out
0	0	0	0 (b)
0	0	1	0 (a)
0	1	0	1 (b)
0	1	1	0 (a)
1	0	0	0 (b)
1	0	1	1 (a)
1	1	0	1 (b)
1	1	1	1 (a)

Bit-Level Multiplexor

 

Arithmetic Logic Unit

 - Combinational logic – a more complex version of a multiplexor
- Control signal selects function computed
- Also computes condition codes
- Example: four function ALU



Memory Elements

- Sequential logic has a memory
- A memory stores data
- The snapshot of the memory is called the state
- A one bit memory is called bistable, that is, it has two internal states
- Flip-flops and latches are implementations of bistables


RS Latch

- An RS latch is a memory element with two inputs: reset (R) and set (S), and two outputs: Q and \overline{Q}

S	R	Q'	\overline{Q}'	comment
0	0	Q	\overline{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	0	0	illegal

where Q' is the next state and Q is the current state.

RS Latch

 

RS Latch State Transition Table

- A state transition table is a way of viewing the operation of an RS latch.


Q	S	R	Q'	comment
0	0	0	0	hold
0	0	1	0	reset
0	1	0	1	set
0	1	1	0	illegal
1	0	0	1	hold
1	0	1	0	reset
1	1	0	1	set
1	1	1	0	illegal

Clocks and Synchronous Circuits

- The RS latch output state changes occur directly in response to changes in the inputs. This is called asynchronous operation.
- Most sequential circuits employ synchronous operation.
 - The output is constrained to change only at a time specified by a global enabling signal
 - This signal is generally called the system clock
- The clock is typically a square wave signal at a particular frequency that imposes order on the state changes.

Gated RS Latch

 - The RS latch can be modified to only change state when a valid enable signal (such as from the system clock) is present.




Registers

- Store a word of data
 - Different from program registers seen in assembly code
- Collection of edge-triggered latches (one for every bit in word)
- Loads input on rising edge of clock


Register Operation

 - Stores data bits
- Generally acts as a barrier between input and output
- As clock rises, loads input




State Machine Example

 - Accumulator circuit
 - Load or accumulate on each cycle



Random-Access Memory

 - Stores multiple words of memory
 - Address input specifies which word to read or write
- Register file
 - Holds values of program registers



Register File Timing

- Reading
 - Like combinational logic
 - Output generated based on input address (after some delay)
- Writing
 - Like register
 - Update only as clock rises

Summary

- Computation
 - Performed by combinational logic
 - Computes Boolean functions
 - Continuously reacts to input changes
- Storage
 - Registers
 - Hold single words
 - Loaded as clock rises
 - Random-access memories
 - Hold multiple words
 - Can have multiple read or write ports
 - Read a word when address input changes
 - Write word as clock rises