

Sequential Implementation

CPSC 235 - Computer Organization

References

- Slides adapted from CMU

Y86-64 Instruction Set

Byte	0	1	2	3	4	5	6	7	8	9
halt	0	0								
nop	1	0								
rrmovq rA, rB	2	0	rA	rB						
irmovq V, rB	3	0	F	rB	V					
rmmovq rA, D(rB)	4	0	rA	rB	D					
mrmovq D(rB), rA	5	0	rA	rB	D					
OPq rA, rB	6	fn	rA	rB						
jXX Dest	7	fn	Dest							
cmovXX rA, rB	2	fn	rA	rB						
call Dest	8	0	Dest							
ret	9	0								
pushq rA	A	0	rA	F						
popq rA	B	0	rA	F						

Building Blocks

- Combinational Logic
 - Compute Boolean functions of inputs
 - Continuously respond to input changes
 - Operate on data and implement control
- Storage Elements
 - Store bits
 - Addressable memories
 - Non-addressable registers
 - Loaded only as clock rises


Sequential Hardware Structure

- State
 - Program counter register (PC)
 - Condition code register (CC)
 - Register file
 - Memories
- Instruction flow
 - Read instruction at address specified by PC
 - Process through stages
 - Update program counter

Sequential Stages

- Fetch: read instruction from memory
- Decode: read program registers
- Execute: compute value or address
- Memory: read or write data
- Write back: write program registers
- PC: update program counter

Sequential Hardware Structure

 

Instruction Decoding

- Instruction format (10 bytes max)
 - Instruction byte: `icode:ifun`
 - Optional register byte: `rA:rB`
 - Optional constant word: `valC`

Executing Arithmetic/Logical Operation

- Fetch: read 2 bytes
- Decode: read operand registers
- Execute: perform operation and set condition codes
- Memory: do nothing
- Write back: update register
- PC update: increment PC by 2

Stage Computation: Arithmetic/Logical Operations

Stage	Op rA rB	Action
Fetch	$icode:ifun = M1[PC]$ $rA:rB = M1[PC+1]$ $valP = PC+2$	read instruction byte read register byte compute next PC
Decode	$valA = R[rA]$ $valB = R[rB]$	read operand A read operand B
Execute	$valE = valB \text{ OP } valA$	Perform ALU operation
Memory		
Write back	$R[rB] = valE$	Write back result
PC update	$PC = valP$	update PC

Executing `rmmovq`

- Fetch: read 10 bytes
- Decode: read operand registers
- Execute: compute effective address
- Memory: write to memory
- Write back: do nothing
- PC update: increment PC by 10

Stage Computation: rmmovq

Stage	rmmovq rA, D(rB)	Action
Fetch	$icode:ifun = M1[PC]$ $rA:rB = M1[PC+1]$ $valC = M8[PC+2]$ $valP = PC+10$	read instruction byte read register byte read 8 byte displacement compute next PC
Decode	$valA = R[rA]$ $valB = R[rB]$	read operand A read operand B
Execute	$valE = valB + valC$	compute effective address (ALU)
Memory	$M8[valE] = valA$	write 8 byte value to memory
Write back		
PC update	$PC = valP$	update PC

Executing popq

- Fetch: read 2 bytes
- Decode: read stack pointer
- Execute: increment stack pointer by 8
- Memory: read from old stack pointer
- Write back: update stack pointer and write result to register
- PC update: increment PC by 2

Stage Computation: popq

Stage	popq rA	Action
Fetch	$\text{icode:ifun} = M1[\text{PC}]$ $\text{rA:rB} = M1[\text{PC}+1]$ $\text{valP} = \text{PC}+2$	read instruction byte read register byte compute next PC
Decode	$\text{valA} = R[\%rsp]$ $\text{valB} = R[\%rsp]$	read stack pointer read stack pointer
Execute	$\text{valE} = \text{valB} + 8$	increment stack pointer (ALU)
Memory	$\text{valM} = M8[\text{valA}]$	read 8 bytes from stack
Write back	$R[\%rsp] = \text{valE}$ $R[\text{rA}] = \text{valM}$	update stack pointer write back result
PC update	$\text{PC} = \text{valP}$	update PC

Executing Conditional Moves

- Fetch: read 2 bytes
- Decode: read operand registers
- Execute: if not condition, then set destination register to 0xF
- Memory: do nothing
- Write back: update register (or not)
- PC update: increment PC by 2

Stage Computation: Conditional Move

Stage	cmovXX rA, rB	Action
Fetch	icode:ifun = M1[PC] rA:rB = M1[PC+1] valP = PC+2	read instruction byte read register byte compute next PC
Decode	valA = R[rA] valB = 0	read operand A read stack pointer
Execute	valE = valB + valA if !Cond(CC,ifun) rB = 0xF	pass val through ALU (v (disable register update)
Memory		
Write back	R[rB] = valE	write back result
PC update	PC = valP	update PC

Executing Jumps

- Fetch: read 9 bytes and increment PC by 9
- Decode: do nothing
- Execute: determine whether to take branch based on jump condition codes
- Memory: do nothing
- Write back: do nothing
- PC update: set PC to destination if branch taken or to incremented PC if not branch

Stage Computation: Jumps

Stage	jXX Dest	Action
Fetch	$\text{icode:ifun} = \text{M1}[\text{PC}]$ $\text{valC} = \text{M8}[\text{PC}+1]$ $\text{valP} = \text{PC}+9$	read instruction byte read 8 byte destination address fall through address
Decode		
Execute	$\text{Cnd} = \text{Cond}(\text{CC}, \text{ifun})$	take branch?
Memory		
Write back		
PC update	$\text{PC} = \text{Cnd} ? \text{valC} : \text{valP}$	update PC

Executing call

- Fetch: read 9 bytes and increment PC by 9
- Decode: read stack pointer
- Execute: decrement stack pointer by 8
- Memory: write incremented PC to new value of stack pointer
- Write back: update stack pointer
- PC update: set PC to Dest

Stage Computation: call

Stage	call Dest	Action
Fetch	$icode:ifun = M1[PC]$ $valC = M8[PC+1]$ $valP = PC+9$	read instruction byte read 8 byte destination address compute return point
Decode	$valB = R[\%rsp]$	read stack pointer
Execute	$valE = valB + -8$	decrement stack pointer (ALU)
Memory	$M8[valE] = valP$	write 8 byte return value on stack
Write back	$R[\%rsp] = valE$	update stack pointer
PC update	$PC = valC$	set PC to destination

Executing ret

- Fetch: read 1 byte
- Decode: read stack pointer
- Execute: increment stack pointer by 8
- Memory: read return address from old stack pointer
- Write back: update stack pointer
- PC update: set PC to return address

Stage Computation: ret

Stage	ret	Action
Fetch	$\text{icode:ifun} = M1[\text{PC}]$	read instruction byte
Decode	$\text{valA} = R[\%rsp]$ $\text{valB} = R[\%rsp]$	read operand stack pointer read operand stack pointer
Execute	$\text{valE} = \text{valB} + 8$	increment stack pointer (ALU)
Memory	$\text{valM} = M8[\text{valA}]$	read return address
Write back	$R[\%rsp] = \text{valE}$	update stack pointer
PC update	$\text{PC} = \text{valM}$	set PC to return address

Computation Steps

Stage	Steps	Action
Fetch	icode:ifun	read instruction byte
	rA, rB	[read register byte]
	valC	[read constant word]
	valP	compute next PC
Decode	valA, srcA	[read operand A]
	valB, srcB	[read operand B]
Execute	valE	perform ALU operation
	Cond code	[set/use condition code]
Memory	valM	[memory read/write]
Write back	dstE	[write back ALU result]
	dstM	[write back memory result]
PC update	PC	update PC

Computed Values

- Fetch

- `icode`: instruction code
- `ifun`: instruction function
- `rA`: instruction register A
- `rB`: instruction register B
- `valC`: instruction constant
- `valP`: incremented PC


Computed Values

- Decode
 - srcA: register ID A
 - srcB: register ID B
 - dstE: destination register E
 - dstM: destination register M
 - valA: register value A
 - valB: register value B

Computed Values

- Execute
 - valE: ALU result
 - Cnd: branch/move flag
- Memory
 - valM: value from memory


Sequential Hardware

 

Sequential Hardware

- Diagram key
 - Blue boxes: pre-designed hardware blocks
 - Gray boxes: control logic
 - White ovals: labels for signals
 - Thick lines: 64-bit word values
 - Thin lines: 4-8 bit values
 - Dotted lines: 1-bit values


Fetch Logic

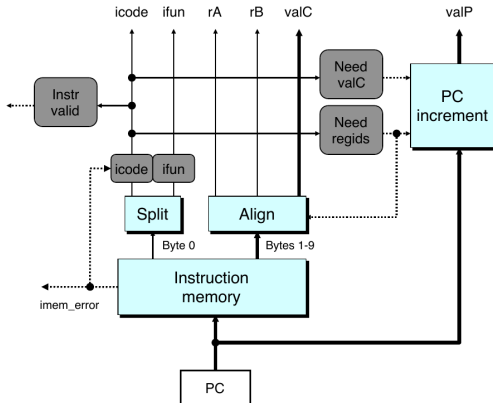

Fetch Logic

- Predefined Blocks
 - PC: Register containing PC
 - Instruction memory: read 10 bytes (PC to PC+9)
 - signal invalid addresses
 - Split: divide instruction byte into `icode` and `ifun`
 - Align: get fields for `rA`, `rB`, and `valC`
- Control Logic
 - Instruction valid: is the instruction valid?
 - `icode`, `ifun`: generate no-op if invalid address
 - Need `regids`: does the instruction have a register byte?
 - Need `valC`: does this instruction have a constant word?


Decode Logic

 

Decode Logic

- Register File
 - Read ports A, B
 - Write ports E, M
 - Addresses are register IDs or 15 (0xF) (no access)
- Control Logic
 - srcA, srcB: read port addresses
 - dstE, dstM: write port addresses
- Signals
 - Cnd: indicate whether or not to perform conditional move (computed in execute stage)


Execute Logic

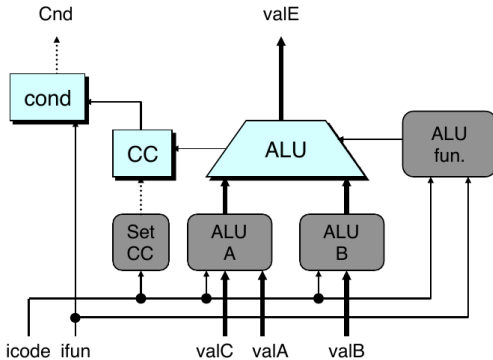

Execute Logic

- Units
 - ALU: implements 4 required functions and generates condition code values
 - CC: register with 3 condition codes
 - cond: computes conditional jump/move flag
- Control Logic
 - Set CC: should condition code register be loaded?
 - ALU A: input A to ALU
 - ALU B: input B to ALU
 - ALU fun: what function should ALU compute?


Memory Logic

 

Memory Logic

- Memory
 - Reads or writes memory word
- Control Logic
 - stat: what is instruction status?
 - Mem. read: should word be read?
 - Mem. write: should word be written?
 - Mem. addr.: select address
 - Mem. data: select data

PC Update Logic

 

- New PC
 - Select next value of PC

Sequential Summary

- Implementation
 - Express every instruction as series of simple steps
 - Follow same general flow for each instruction type
 - Assemble registers, memories, pre-designed combinational blocks
 - Connect with control logic
- Limitations
 - Too slow to be practical
 - In one cycle must propagate through instruction memory, register file, ALU, and data memory
 - Would need to run the clock very slowly
 - Hardware units only active for fraction of clock cycle